

# LecLabMeet-12-MIPS-vhdl

a walkthrough  
part-1-and-2

**Sachin B. Patkar**

**EE-705-spring-sem-2020-21 VLSI Design Lab**  
Mon-22-Feb-2021

Based on

<https://www.fpga4student.com/2017/09/vhdl-code-for-mips-processor.html>

ISA, uArch etc

The Instruction Format and [Instruction Set Architecture](https://www.fpga4student.com) for the 16-bit single-cycle MIPS are as follows:

Name	Fields					Comments
Field size	3 bits	3 bits	3 bits	3 bits	4 bits	All MIPS-L instructions 16 bits
R-format	op	rs	rt	rd	funct	Arithmetic instruction format
I-format	op	rs	rt	Address/immediate		Transfer, branch, immediate format
J-format	op	target address				Jump instruction format

Name	Format	Example					Comments
		3 bits	3 bits	3 bits	3 bits	4 bits	
add	R	0	2	3	1	0	add \$1,\$2,\$3
sub	R	0	2	3	1	1	sub \$1,\$2,\$3
and	R	0	2	3	1	2	and \$1,\$2,\$3
or	R	0	2	3	1	3	or \$1,\$2,\$3
slt	R	0	2	3	1	4	slt \$1,\$2,\$3
jr	R	0	7	0	0	8	jr \$7
lw	I	4	2	1	7		lw \$1, 7 (\$2)
sw	I	5	2	1	7		sw \$1, 7 (\$2)
beq	I	6	1	2	7		beq \$1,\$2, 7
addi	I	7	2	1	7		addi \$1,\$2, 7
j	J	2	500				j 1000
jal	J	3	500				jal 1000
slti	I	1	2	1	7		slti \$1,\$2, 7

# MIPS Processor

PC

Register File

Data  
Memory

Instruction  
Memory

ALU

[fpga4student.com](http://fpga4student.com)


1. Add :  $R[rd] = R[rs] + R[rt]$
2. Subtract :  $R[rd] = R[rs] - R[rt]$
3. And:  $R[rd] = R[rs] \& R[rt]$
4. Or :  $R[rd] = R[rs] | R[rt]$
5. SLT:  $R[rd] = 1$  if  $R[rs] < R[rt]$  else 0
6. Jr:  $PC=R[rs]$
7. Lw:  $R[rt] = M[R[rs]+SignExtImm]$
8. Sw :  $M[R[rs]+SignExtImm] = R[rt]$
9. Beq : if( $R[rs]==R[rt]$ )  $PC=PC+1+BranchAddr$
10. Addi:  $R[rt] = R[rs] + SignExtImm$
11. J :  $PC=JumpAddr$
12. Jal :  $R[7]=PC+2; PC=JumpAddr$
13. SLTI:  $R[rt] = 1$  if  $R[rs] < imm$  else 0

**Caution :** A couple of minor discrepancies between the (register-transfer-notation) RTN description of instructions and their actual implementation in fpga4student's vhdl code

$SignExtImm = \{ 9\{immediate[6]\}, imm$

$JumpAddr = \{ (PC+1)[15:13], address\}$

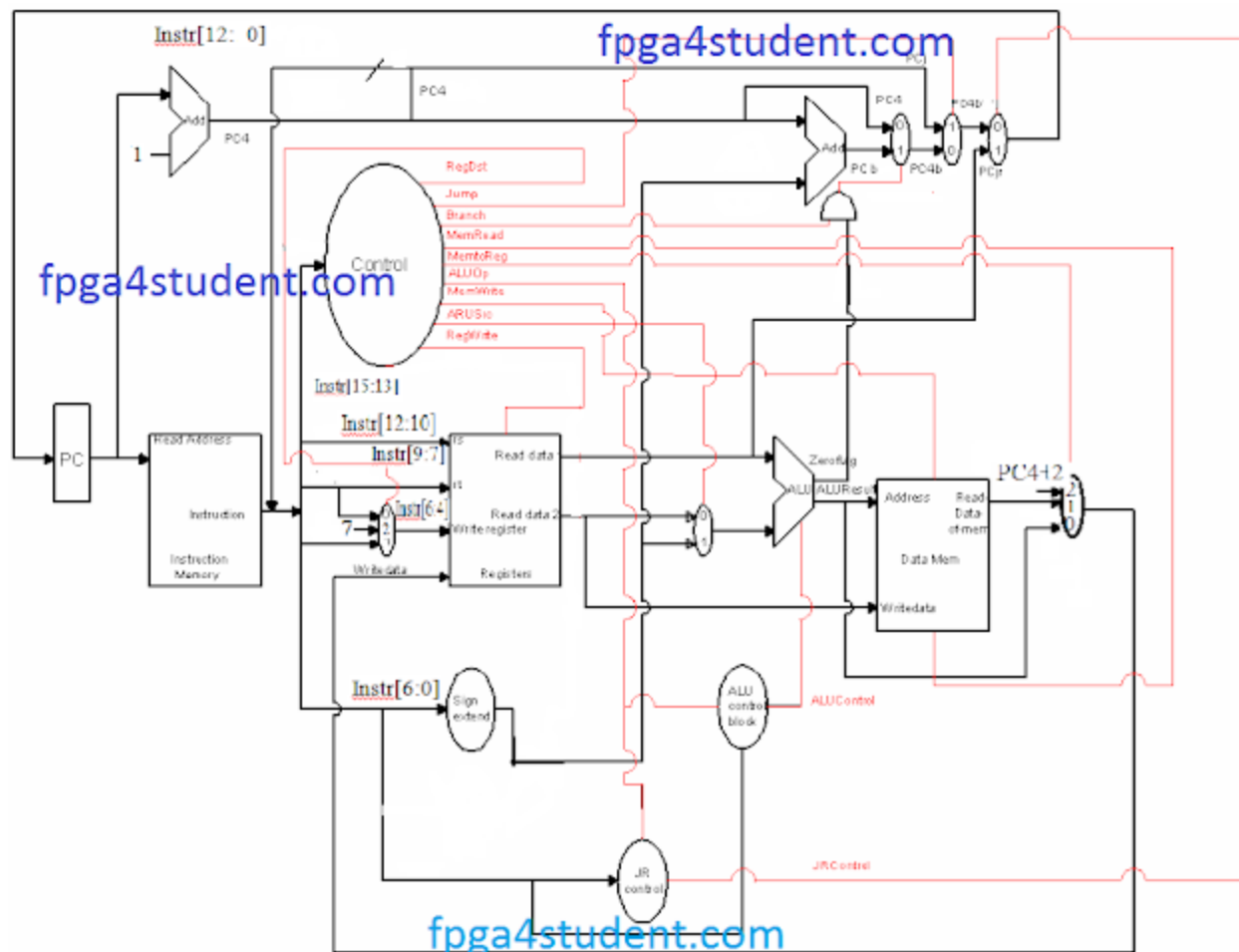$BranchAddr = \{ 7\{immediate[6]\}, immediate, 1'b0 \}$



Let's correlate  
HDL code fragments  
with  
parts of Microarchitecture !



-- PC of the MIPS Processor in VHDL

```
process(clk,reset) begin
  if (reset='1') then pc_current <= x"0000";
  elsif (rising_edge(clk)) then pc_current <= pc_next;
  end if;
end process;
```

-- PC + 2

```
pc2 <= pc_current + x"0002";
```


- PC is assumed to contain byte-address, -
- and not word address, hence +2

Instruction\_Memory: **entity work**.Instruction\_Memory\_VHDL


```
port map ( pc=> pc_current, instruction=> instr );
```

control: **entity work**.control\_unit\_VHDL
 
```
port map (reset=> reset, opcode=> instr(15 downto 13),
  reg_dst=> reg_dst, mem_to_reg=> mem_to_reg,
  alu_op=> alu_op, jump=> jump, branch=> branch, mem_read=> mem_read,
  mem_write=> mem_write, alu_src=> alu_src,
  reg_write=> reg_write, sign_or_zero=> sign_or_zero );
```



 Note however PC(k downto 1) would be used to address  $2^{**}k$  2-byte-wides-words of InstrROM



```

entity register_file_VHDL is port ( clk,rst: in std_logic; reg_write_en: in std_logic;
reg_write_dest: in std_logic_vector(2 downto 0);
reg_write_data: in std_logic_vector(15 downto 0); reg_read_addr_1: in std_logic_vector(2 downto 0);
reg_read_data_1: out std_logic_vector(15 downto 0); reg_read_addr_2: in std_logic_vector(2 downto 0);
reg_read_data_2: out std_logic_vector(15 downto 0)
);

```

```

end register_file_VHDL;

```

```

architecture Behavioral of register_file_VHDL is

```

```

    type reg_type is array (0 to 7 ) of std_logic_vector (15 downto 0);

```

```

    signal reg_array: reg_type;

```

```

begin

```

```

    process(clk,rst) begin      if(rst='1') then .....

```

```

        elsif(rising_edge(clk)) then

```

```

            if(reg_write_en='1') then

```

```

                reg_array(to_integer(unsigned(reg_write_dest))) <= reg_write_data;

```

```

            end if;

```

```

        end if;

```

```

    end process;

```

```

    reg_read_data_1 <= x"0000" when reg_read_addr_1 = "000" else

```

```

        reg_array(to_integer(unsigned(reg_read_addr_1)));

```

```

    reg_read_data_2 <= x"0000" when reg_read_addr_2 = "000" else

```

```


        reg_array(to_integer(unsigned(reg_read_addr_2)));

```

```


end Behavioral;

```

 


Walking along the Datapath

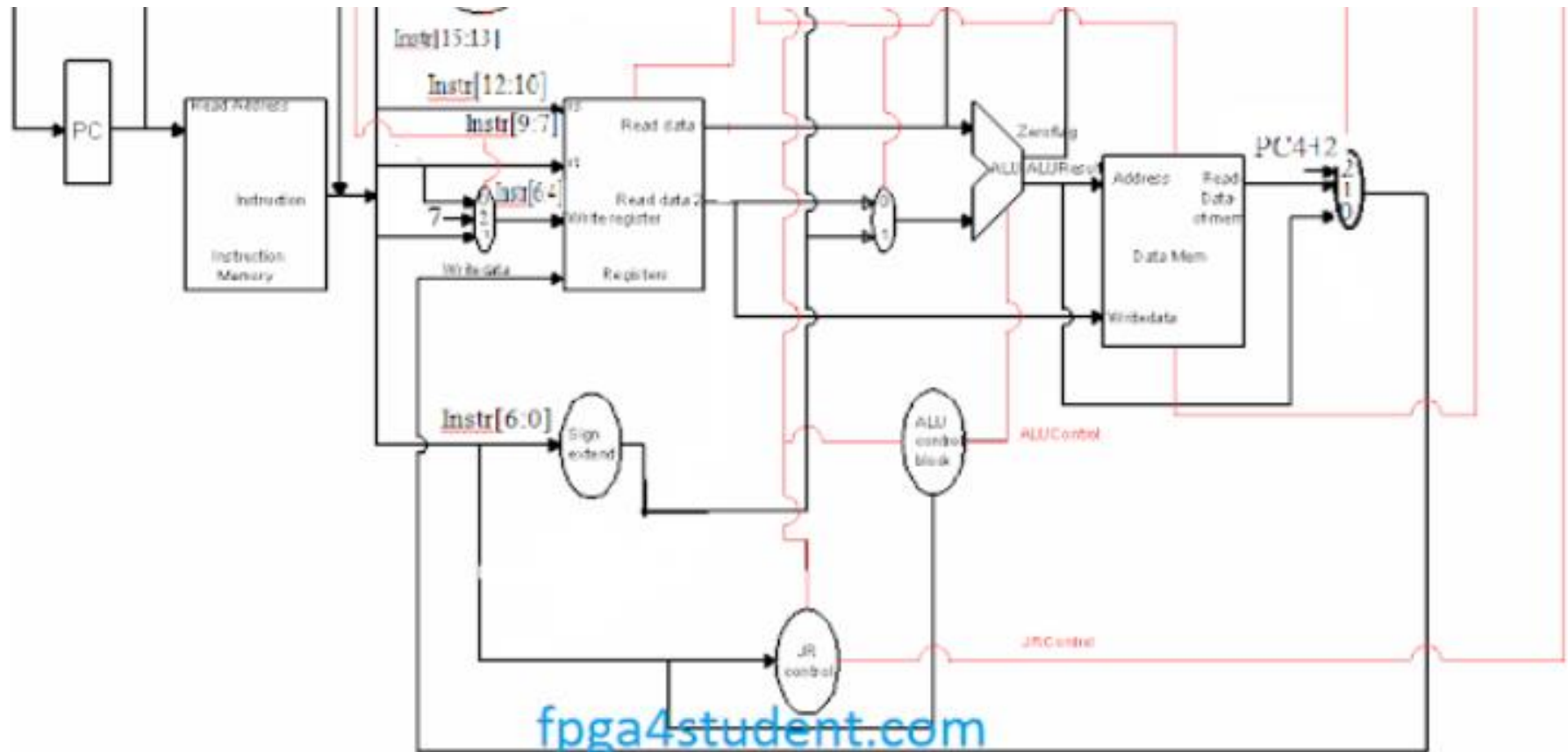
To help focus on the arithm/memory instructions, I have omitted branch/jump related microarchitecture from the diagram




# R-type instruction

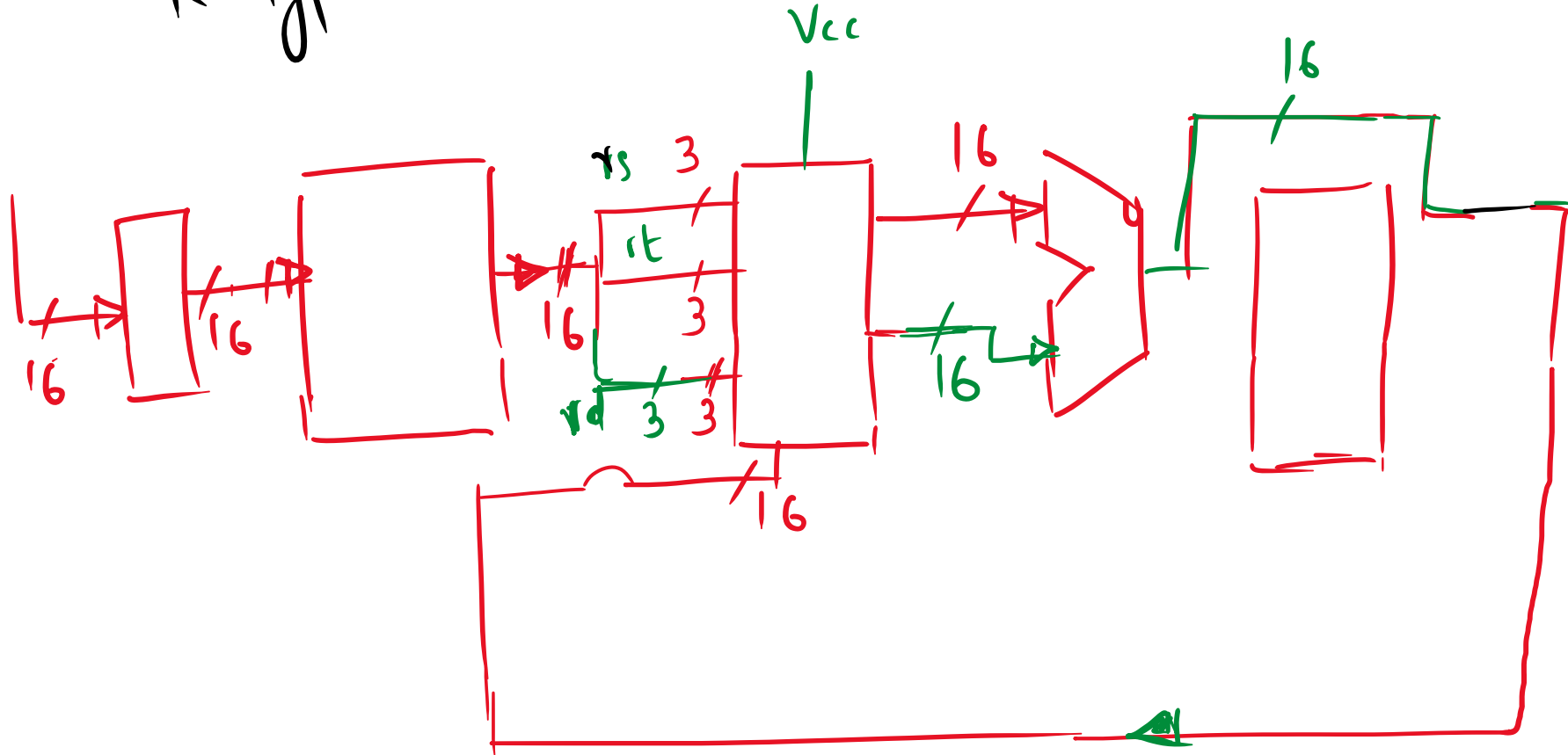

# ADD - immediate

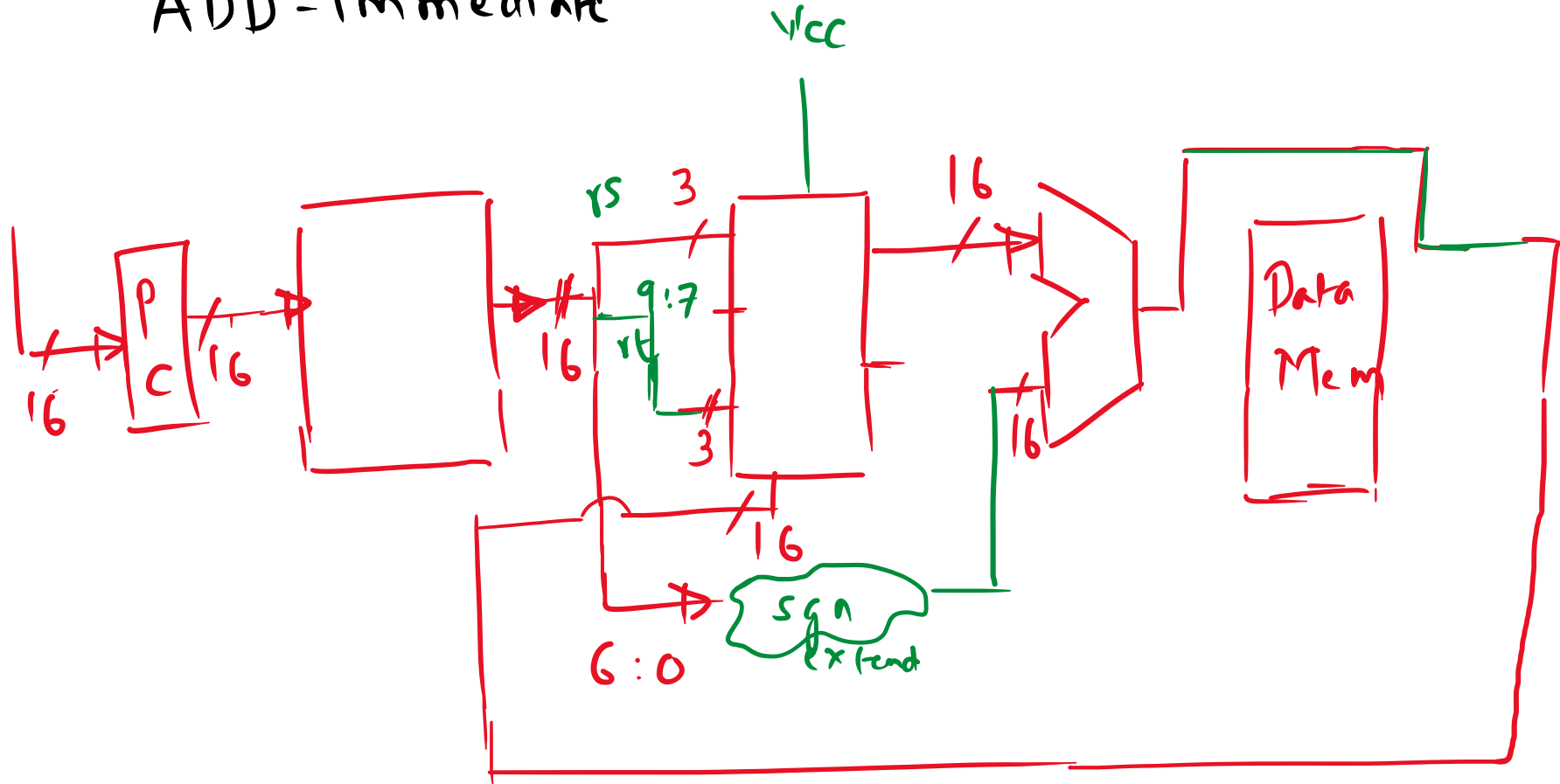


# Load Word

 





# Store Word

 

# Juxtaposing ....

 

 


1. Add :  $R[rd] = R[rs] + R[rt]$
2. Subtract :  $R[rd] = R[rs] - R[rt]$
3. And:  $R[rd] = R[rs] \& R[rt]$
4. Or :  $R[rd] = R[rs] | R[rt]$
5. SLT:  $R[rd] = 1$  if  $R[rs] < R[rt]$  else 0
6. Jr:  $PC=R[rs]$
7. Lw:  $R[rt] = M[R[rs]+SignExtImm]$
8. Sw :  $M[R[rs]+SignExtImm] = R[rt]$
9. Beq : if( $R[rs]==R[rt]$ )  $PC=PC+1+BranchAddr$
10. Addi:  $R[rt] = R[rs] + SignExtImm$
11. J :  $PC=JumpAddr$
12. Jal :  $R[7]=PC+2; PC=JumpAddr$
13. SLTI:  $R[rt] = 1$  if  $R[rs] < imm$  else 0
 



$SignExtImm = \{ 9\{immediate[6]\}, imm$   
 $JumpAddr = \{ (PC+1)[15:13], address\}$   
 $BranchAddr = \{ 7\{immediate[6]\}, immediate, 1'b0 \}$

RTN  
Register Transfer  
Notation  
for description of  
Datapath

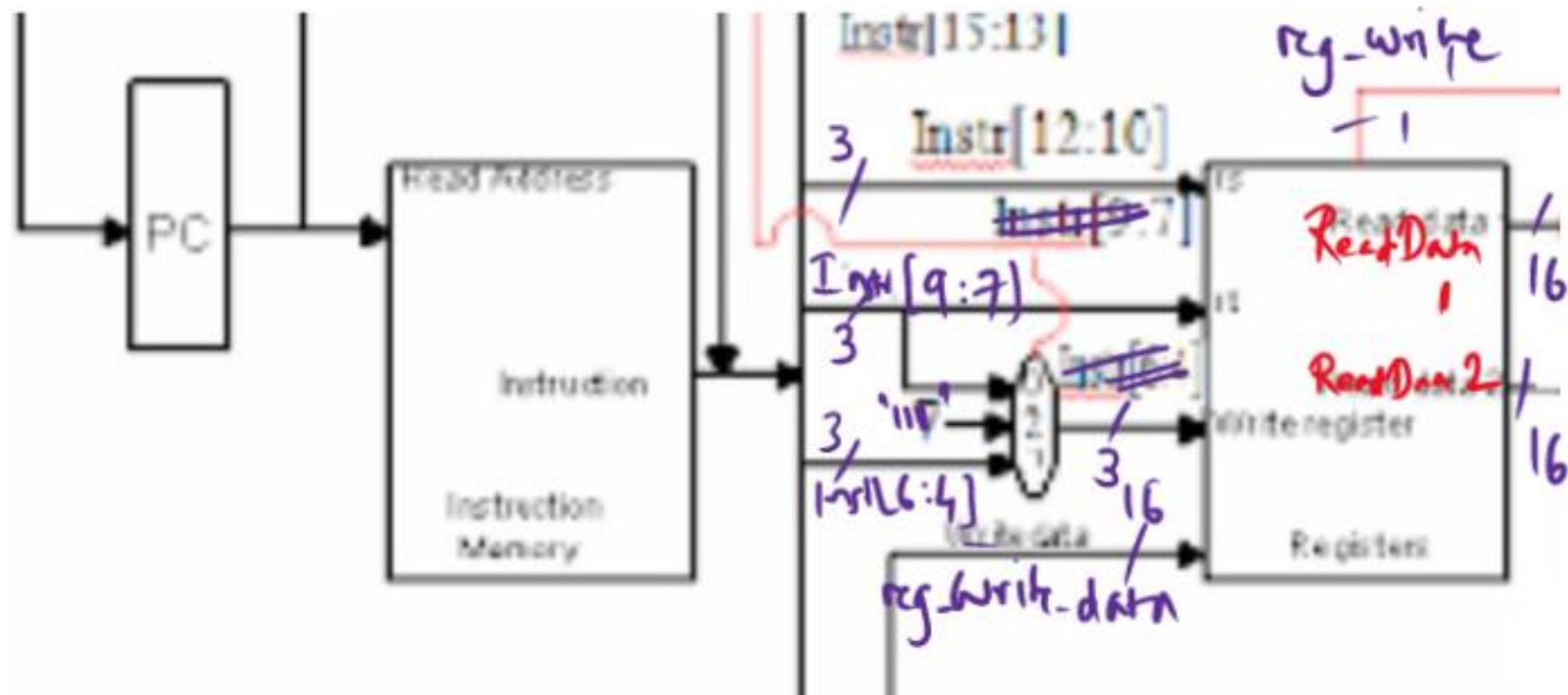**Caution : Mismatch between this RTN description and the implementation. Here  $PC+1$  Indicates the address of next instruction-word ( not byte ). Whereas in HDL code, it is assumed that PC contains address of first byte of instruction**


Note the corrections : The rs field of Instr, i.e. Instr[12:10] is fed to reg\_read\_addr\_1 port of RegFile, rt field, i.e. Instr[9:7] drives the 2nd address port of RegFile. And both rt and rd ( i.e. Instr[6:4] ) fields of Instr, along with constant "111" are options for the 3rd address port of RegFile



 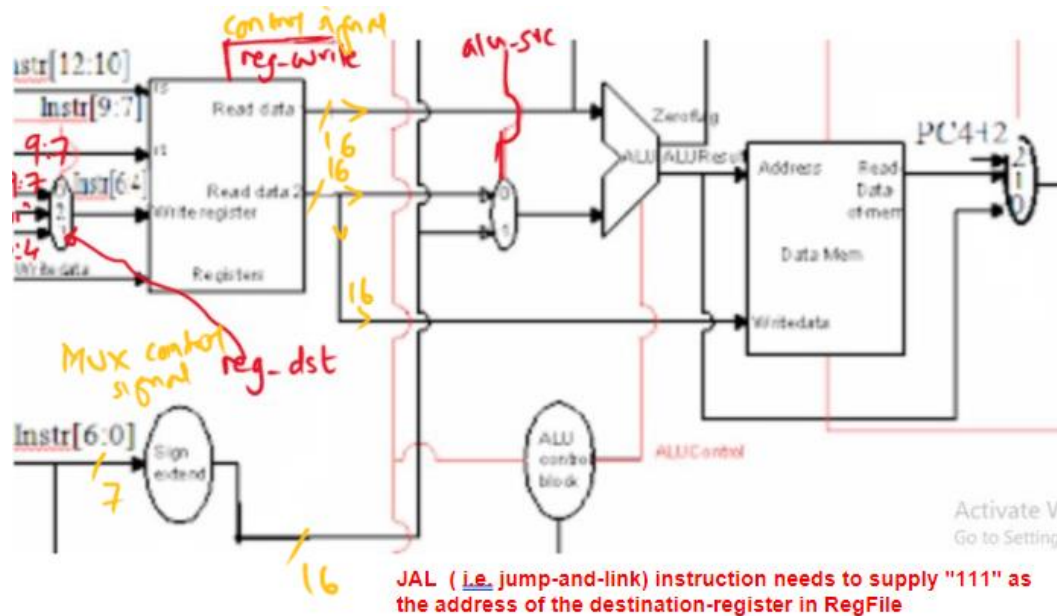

**JAL ( i.e. jump-and-link) insruction needs to supply "111" as the address of the destination-register in RegFile**

**Let's Look at Some Control Signals !**

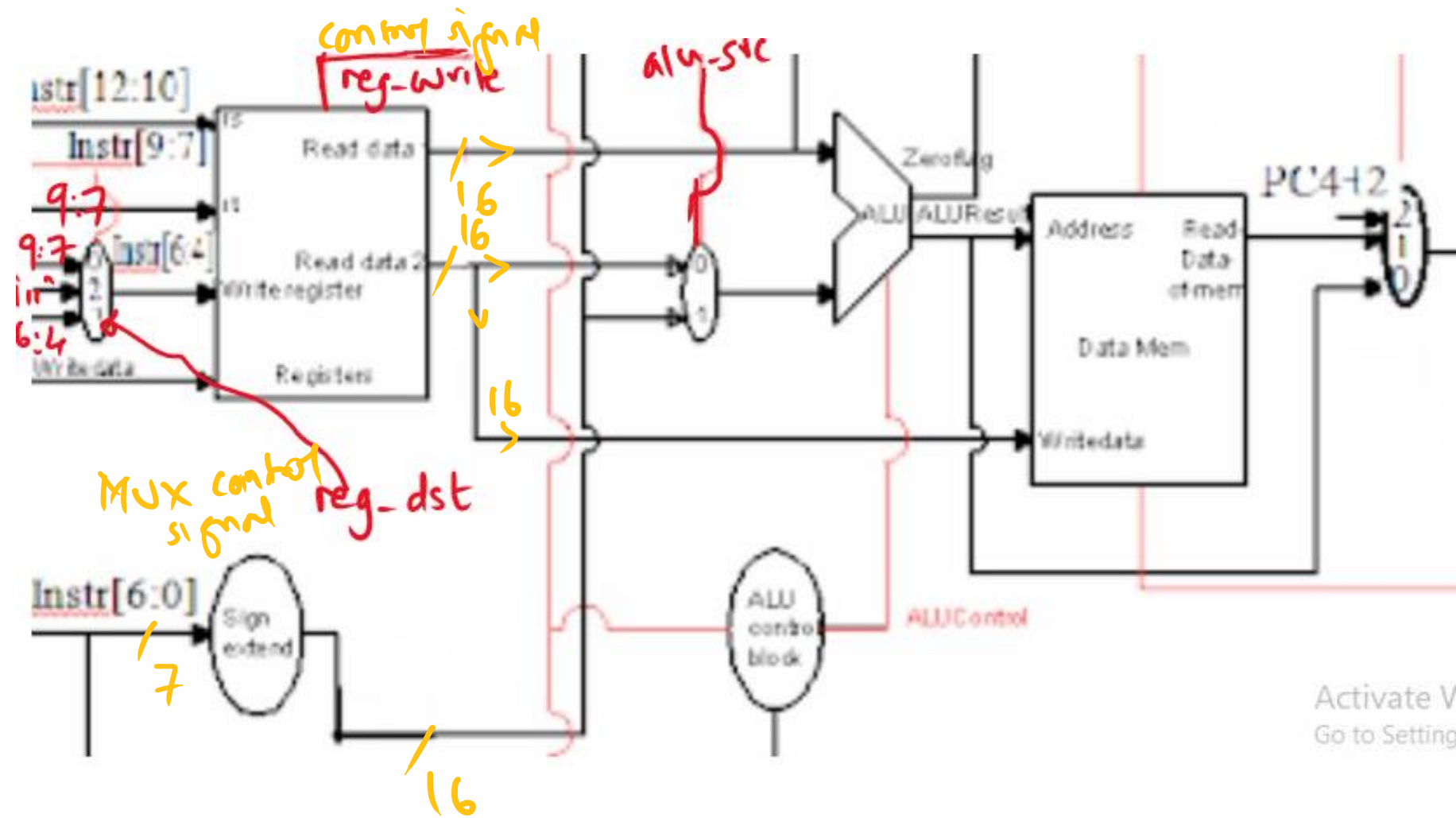

Activate V  
Go to Setting



For any R-type instruction  $rt$  rd field  $inst[6:4]$  reg-dst = 01


reg-write = 1



Based on the provided instruction set, the data-path and control unit are designed and implemented.

Control unit design:

Instruction	Control signals								
	Reg Dst	ALU Src	Memto Reg	Reg Write	MemRead	Mem Write	Branch	ALUOp	Jump
R-type	1	0	0	1	0	0	0	00	0
LW	0	1	1	1	1	0	0	11	0
SW	0	1	0	0	0	1	0	11	0
addi	0	1	0	1	0	0	0	11	0
beq	0	0	0	0	0	0	1	01	0
j	0	0	0	0	0	0	0	00	1
jal	2	0	2	1	0	0	0	00	1
slli	0	1	0	1	0	0	0	10	0

 


aluSrc = 0


Based on the provided instruction set, the data-path and control unit are designed and implemented.

Control unit design:

Control signals									
Instruction	Reg Dst	ALU Src	Memto Reg	Reg Write	MemRead	Mem Write	Branc h	ALUOp	Jump
R-type	1	0	0	1	0	0	0	00	0
LW	0	1	1	1	1	0	0	11	0
SW	0	1	0	0	0	1	0	11	0
addi	0	1	0	1	0	0	0	11	0
beq	0	0	0	0	0	0	1	01	0
j	0	0	0	0	0	0	0	00	1
jal	2	0	2	1	0	0	0	00	1
slti	0	1	0	1	0	0	0	10	0

alu-src

 

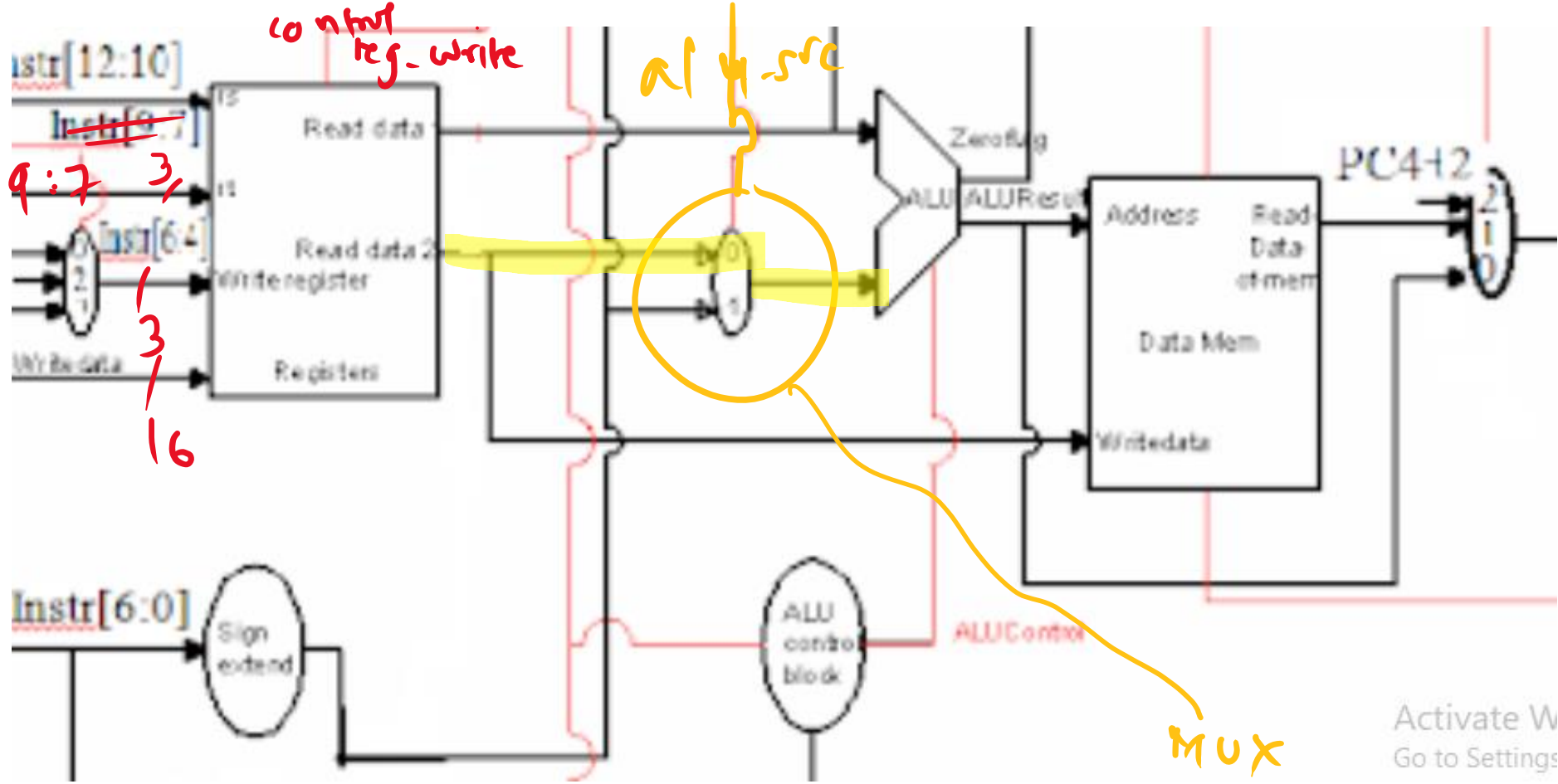

Activate W  
Go to Settings

Based on the provided instruction set, the data-path and control unit are designed and implemented.

Control unit design:

Control signals									
Instruction	Reg Dst	ALU Src	Memto Reg	Reg Write	MemRead	Mem Write	Branc h	ALUOp	Jump
R-type	1	0	0	1	0	0	0	00	0
LW	0	1	1	1	1	0	0	11	0
SW	0	1	0	0	0	1	0	11	0
addi	0	1	0	1	0	0	0	11	0
beq	0	0	0	0	0	0	1	01	0
j	0	0	0	0	0	0	0	00	1
jal	2	0	2	1	0	0	0	00	1
slti	0	1	0	1	0	0	0	10	0


  
 Alu-5bit
   
 Immediate
   
 Operand
   
 (after
   
 sign/zero
   
 extension)



- We would need either sign-extended version of zero-extended version
- of "imm" field ( i.e. instr(6 downto 0) ) for I-format arithmetic (add/sub) or I-format logical-op instruction

```
tmp1 <= (others => instr(6));
```

```
sign_ext_im <= tmp1 & instr(6 downto 0);
```

```
zero_ext_im <= "0000000000"& instr(6 downto 0);
```

```
imm_ext <= sign_ext_im when sign_or_zero='1' else zero_ext_im;
```

- this sign/zero extended version of instr(6 downto 0) gets routed to the
- 2nd input of ALU as an alternative to the 2nd 16-bit-wide output of RF

```
read_data2 <= imm_ext when alu_src='1' else reg_read_data_2;
```



Based on the provided instruction set, the data-path and control unit are designed and implemented.

Control unit design:

Control signals									
Instruction	Reg Dst	ALU Src	Memto Reg	Reg Write	MemRead	Mem Write	Branc h	ALUOp	Jump
R-type	1	0	0	1	0	0	0	00	0
LW	0	1	1	1	1	0	0	11	0
SW	0	1	0	0	0	1	0	11	0
addi	0	1	0	1	0	0	0	11	0
beq	0	0	0	0	0	0	1	01	0
j	0	0	0	0	0	0	0	00	1
jal	2	0	2	1	0	0	0	00	1
slti	0	1	0	1	0	0	0	10	0

A Closer Look at the Register File  
in this VHDL model



```

entity register_file_VHDL is port ( clk_rst: in std_logic; reg_write_en: in std_logic;
reg_write_dest: in std_logic_vector(2 downto 0);
reg_write_data: in std_logic_vector(15 downto 0); reg_read_addr_1: in std_logic_vector(2 downto 0);
reg_read_data_1: out std_logic_vector(15 downto 0); reg_read_addr_2: in std_logic_vector(2 downto 0);
reg_read_data_2: out std_logic_vector(15 downto 0)
);

```

architecture Behavioral of register\_file\_VHDL is

```

type reg_type is array (0 to 7) of std_logic_vector(15 downto 0);

```

```

signal reg_array: reg_type;

```

begin

```

process(clk_rst) begin if(rst='1') then .....

```

```

elseif(rising_edge(clk)) then

```

```

if(reg_write_en='1') then

```

```

reg_array(to_integer(unsigned(reg_write_dest))) <= reg_write_data;

```

```

end if;

```

```

end if;

```

```

end process;

```

```

reg_read_data_1 <= x"0000" when reg_read_addr_1 = "000" else

```

```

reg_array(to_integer(unsigned(reg_read_addr_1)));

```

```

reg_read_data_2 <= x"0000" when reg_read_addr_2 = "000" else

```

```


reg_array(to_integer(unsigned(reg_read_addr_2)));

```

```



end Behavioral;

```

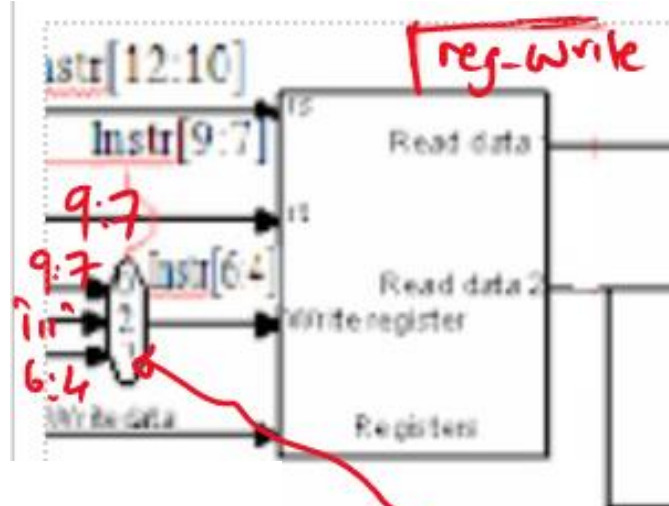

register\_file: **entity work**.register\_file\_VHDL **port map**
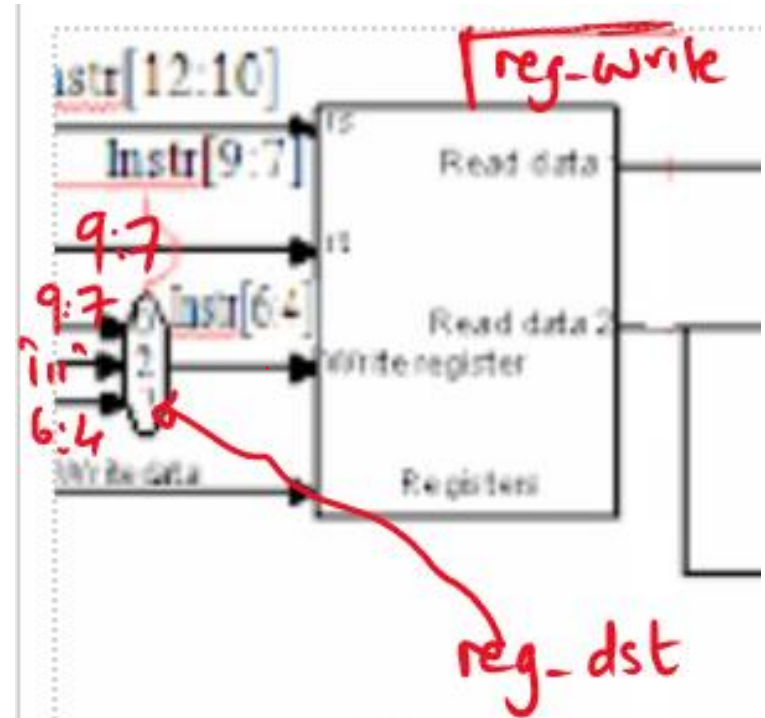 
```
( clk => clk, rst => reset, reg_write_en => reg_write,  
  reg_write_dest => reg_write_dest, reg_write_data => reg_write_data,  
  reg_read_addr_1 => reg_read_addr_1, reg_read_data_1 => reg_read_data_1,  
  reg_read_addr_2 => reg_read_addr_2, reg_read_data_2 => reg_read_data_2 );
```




register\_file: **entity** **work**.register\_file\_VHDL **port map**

( clk => clk, rst => reset, reg\_write\_en => reg\_write)

reg\_write\_dest => reg\_write\_dest, reg\_write\_data => reg\_write\_data,

reg\_read\_addr\_1 => reg\_read\_addr\_1, reg\_read\_data\_1 => reg\_read\_data\_1,


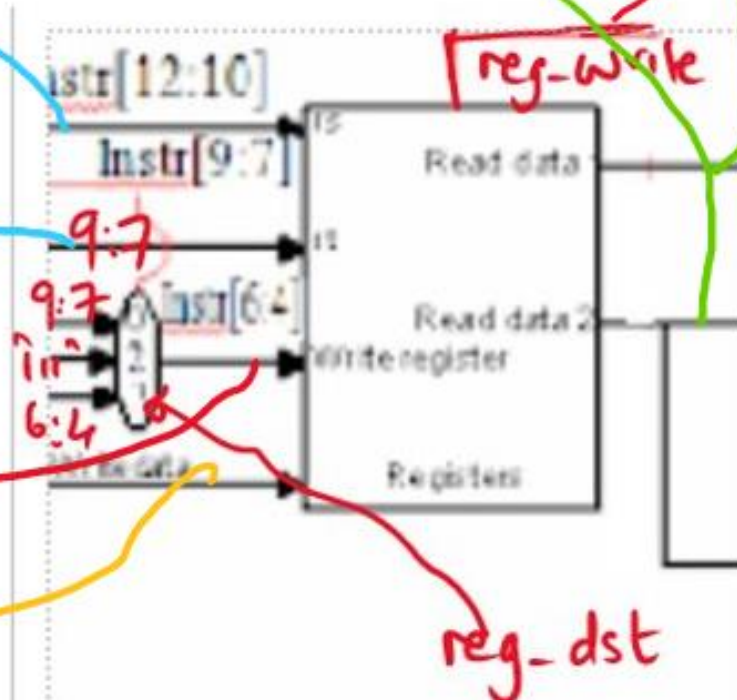
reg\_read\_addr\_2 => reg\_read\_addr\_2, reg\_read\_data\_2 => reg\_read\_data\_2 );



```

reg_write_dest <= "111" when reg_dst = "10" else
instr(6 downto 4) when reg_dst = "01" else
instr(9 downto 7);

```

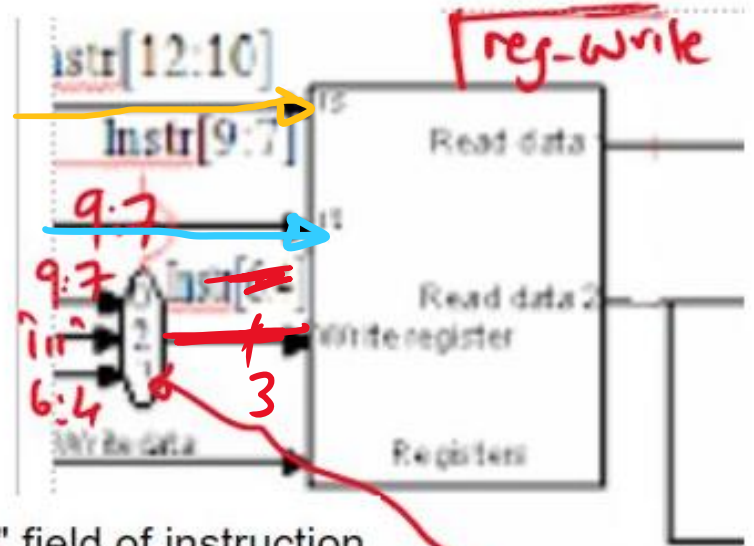 

```

reg_read_addr_1 <= instr(12 downto 10); -- "rs" field of instruction

```

```

reg_read_addr_2 <= instr(9 downto 7); -- "rt" field of instruction

```

- this pair of 3-bit wide signals are used for selecting
- 2 registers from `RegFile` for read-out
- at the pair of 16-bit-wide output ports of the `RegFile`

```
reg_write_dest <= "111" when reg_dst= "10" else
    instr(6 downto 4) when reg_dst= "01" else
    instr(9 downto 7);
```

- as indicated during LecMeet-11 Thu-18-Feb21
- reg\_write\_dest is output of a 3-bit-wide 3-way multiplexer
- it chooses either instr(9 downto 7) ( namely, the "rt" field of instruction )
- or instr(6 downto 4) ( namely, the "rd" field )
- or "111" respectively for
- the following settings of "reg\_dst" , namely "00","01","10"

```
reg_read_addr_1 <= instr(12 downto 10); -- "rs" field of instruction
reg_read_addr_2 <= instr(9 downto 7);   -- "rt" field of instruction
-- this pair of 3-bit wide signals are used for selecting
-- 2 registers from RegFile for read-out
-- at the pair of 16-bit-wide output ports of the RegFile
```





```

process(clk,rst) begin    if(rst='1') then .....
    elsif(rising_edge(clk)) then
        if(reg_write_en='1') then
            reg_array(to_integer(unsigned(reg_write_dest))) <= reg_write_data;
        end if;
    end if;
end process;

```

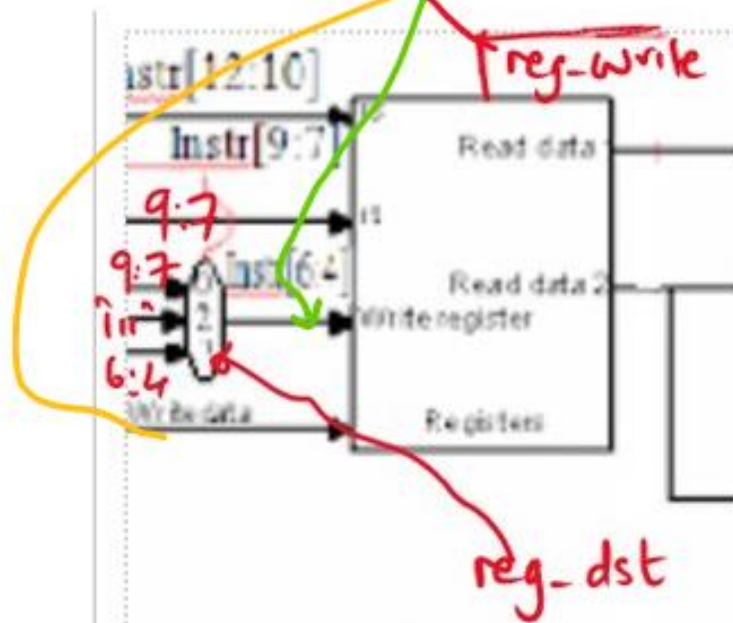vhdl  
modeling  
of write operation  
inside RegFile



 

```

reg_read_data_1 <= x"0000" when reg_read_addr_1 = "000" else
    reg_array(to_integer(unsigned(reg_read_addr_1)));
reg_read_data_2 <= x"0000" when reg_read_addr_2 = "000" else
    reg_array(to_integer(unsigned(reg_read_addr_2)));
  
```


```

reg_read_data_1 <= x"0000" when reg_read_addr_1 = "000" else
reg_array(to_integer(unsigned(reg_read_addr_1)));
reg_read_data_2 <= x"0000" when reg_read_addr_2 = "000" else
reg_array(to_integer(unsigned(reg_read_addr_2)));

```

array of registers

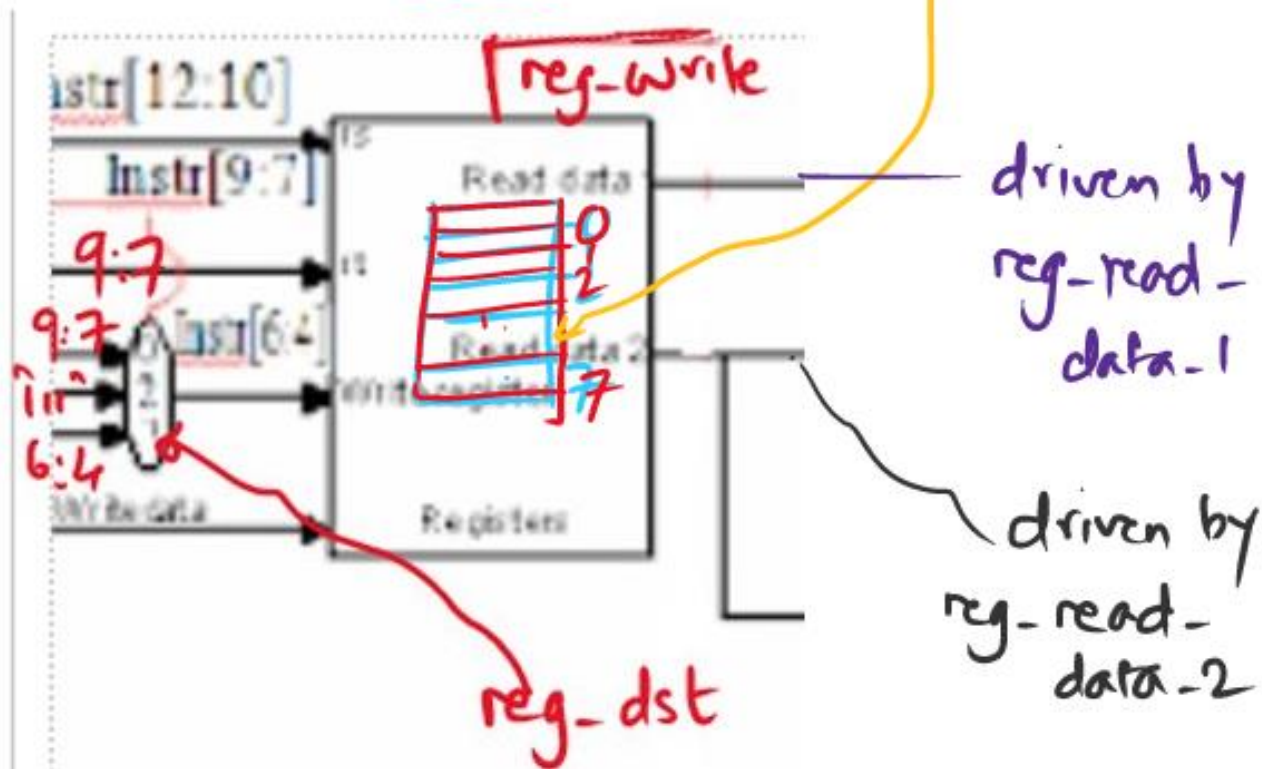The  
Read Out  
logic of  
Register  
File






```


reg_read_data_1 <= x"0000" when reg_read_addr_1 = "000" else
reg_array(to_integer(unsigned(reg_read_addr_1)));
reg_read_data_2 <= x"0000" when reg_read_addr_2 = "000" else
reg_array(to_integer(unsigned(reg_read_addr_2)));

```

array of registers

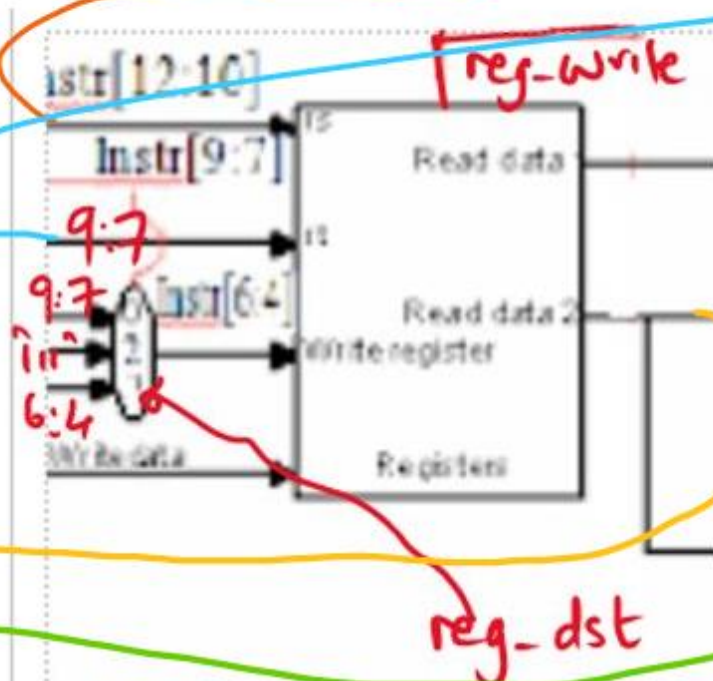

# WriteBack Portion of Datapath

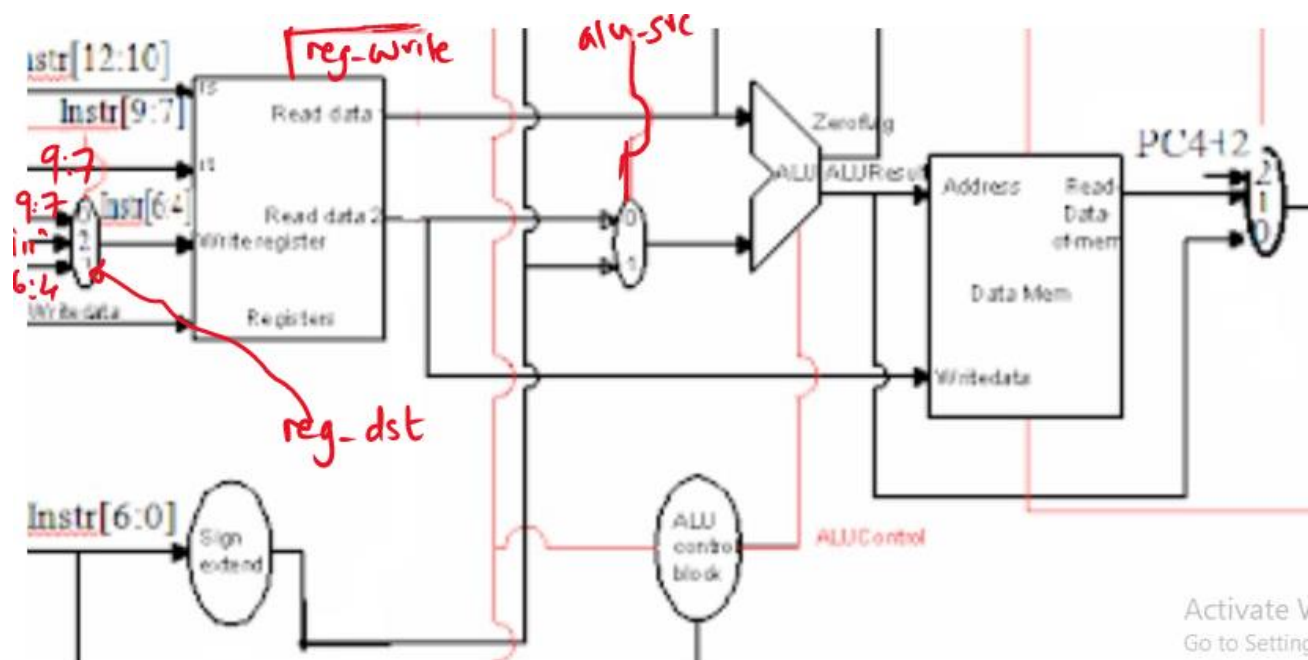

Activate V  
Go to Setting


-- write back of the MIPS Processor in VHDL

```
reg_write_data <= pc2 when (mem_to_reg = "10") else  
    mem_read_data when (mem_to_reg = "01") else  
    ALU_out;
```

```
pc_out <= pc_current;
```

```
alu_result <= ALU_out;
```

*ignore*

 


-- write back of the MIPS Processor in VHDL


```
reg_write_data <= pc2 when (mem_to_reg = "10") else  
  mem_read_data when (mem_to_reg = "01") else  
  ALU_out;
```

```
pc_out <= pc_current;
```

```
alu_result <= ALU_out;
```

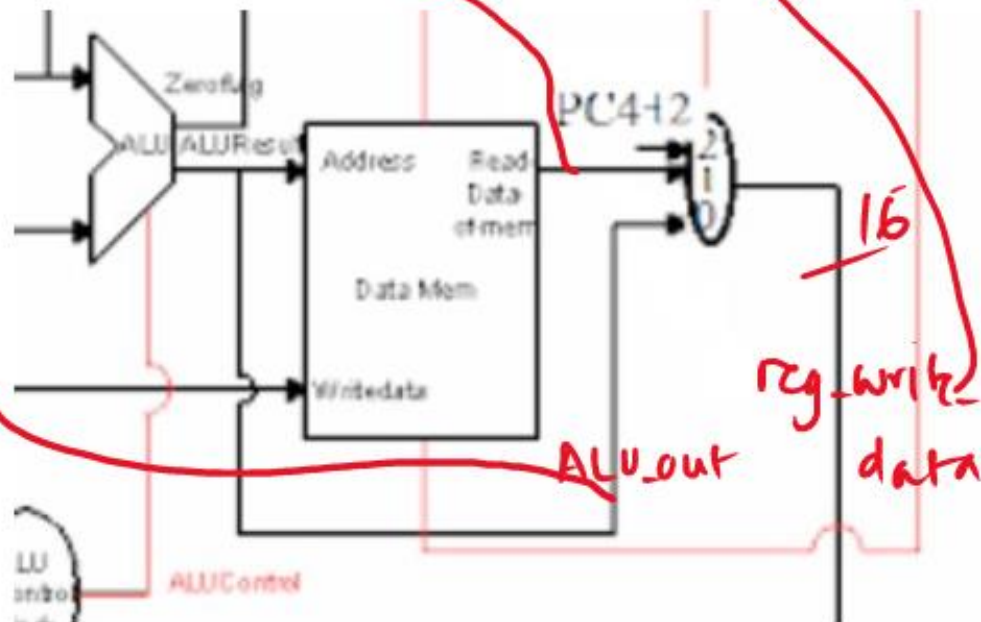

# Data Memory model in VHDL

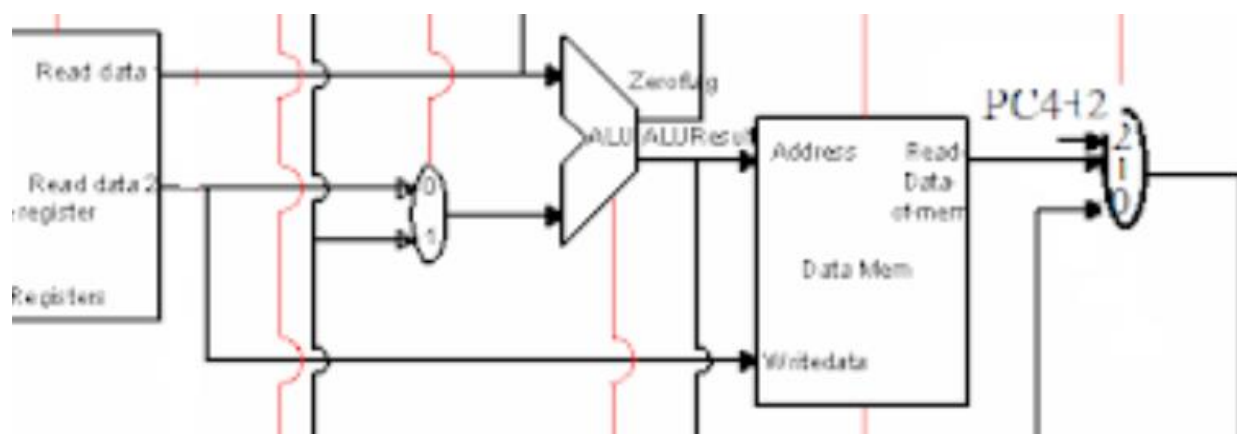

```
-- data memory of the MIPS Processor in VHDL
data_memory: entity work.Data_Memory_VHDL port map
(
  clk => clk,
  mem_access_addr => ALU_out,
  mem_write_data => reg_read_data_2,
  mem_write_en => mem_write,
  mem_read => mem_read,
  mem_read_data => mem_read_data
);

-- write back of the MIPS Processor in VHDL
reg_write_data <= pc2 when (mem_to_reg = "10") else
  mem_read_data when (mem_to_reg = "01") else ALU_out;
```

```

entity Data_Memory_VHDL is
port (
  clk: in std_logic;
  mem_access_addr: in std_logic_Vector(15 downto 0);
  mem_write_data: in std_logic_Vector(15 downto 0);
  mem_write_en, mem_read: in std_logic;
  mem_read_data: out std_logic_Vector(15 downto 0)
);
end Data_Memory_VHDL;

architecture Behavioral of Data_Memory_VHDL is
  signal i: integer;
  signal ram_addr: std_logic_vector(7 downto 0);
  type data_mem is array (0 to 255) of std_logic_vector (15 downto 0);
  signal RAM: data_mem := ((others=> (others=>'0')));
begin

  ram_addr <= mem_access_addr(8 downto 1);
  process(clk)
  begin
    if(rising_edge(clk)) then
      if (mem_write_en='1') then
        ram(to_integer(unsigned(ram_addr))) <= mem_write_data;
      end if;
    end if;
  end process;
  mem_read_data <= ram(to_integer(unsigned(ram_addr))) when (mem_read='1') else :

end Behavioral;

```

Here too, as in case of Program Counter PC, the address is assumed to be of "byte" in the memory.

Since this memory is an array of  $2^{**}8$  2-byte-wide datawords, we use bits 8 downto 1 of the address





**architecture Behavioral of Data\_Memory\_VHDL is**

**signal** i: **integer**;

**signal** ram\_addr: **std\_logic\_vector**(**7** **downto** **0**);

**type** data\_mem **is array** (**0** **to** **255** ) **of** **std\_logic\_vector** (**15** **downto** **0**);

**signal** RAM: data\_mem :=((**others**=> (**others**=>'0')));

**begin**

ram\_addr <= mem\_access\_addr(**8** **downto** **1**);

**process**(clk) **begin**

**if**(rising\_edge(clk)) **then**

**if** (mem\_write\_en='1') **then**

ram(to\_integer(unsigned(ram\_addr))) <= mem\_write\_data;

**end if**;


**end if**;

**end process**;

mem\_read\_data <= ram(to\_integer(unsigned(ram\_addr)))


**when** (mem\_read='1') **else** x"0000";

**end Behavioral** ;

 

```
ram_addr <= mem_access_addr(8 downto 1);  
process(clk) begin  
    if(rising_edge(clk)) then  
        if (mem_write_en='1') then  
            ram(to_integer(unsigned(ram_addr))) <= mem_write_data;  
        end if;  
    end if;  
end process;  
mem_read_data <= ram(to_integer(unsigned(ram_addr)))  
                    when (mem_read='1') else x"0000";
```

# Branch/Jump Circuit

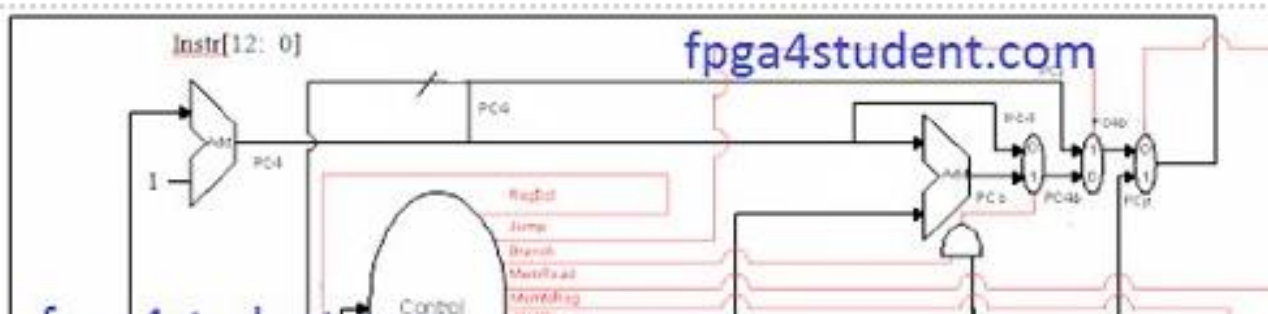

```
im_shift_1 <= imm_ext(14 downto 0) & '0'; -- immediate shift 1
```

```
no_sign_ext <= (not im_shift_1) + x"0001";
```

```
PC_beg <= (pc2 - no_sign_ext) when im_shift_1(15) = '1' else (pc2 + im_shift_1);
```

```
beq_control <= branch and zero_flag; -- beq control
```

```
PC_4beq <= PC_beg when beq_control='1' else pc2; -- PC_beg
```

```
jump_shift_1 <= instr(13 downto 0) & '0'; -- jump shift left 1
```

```
PC_j <= pc2(15) & jump_shift_1; -- PC_j
```

```
PC_4beqj <= PC_j when jump = '1' else PC_4beq; -- PC_4beqj
```

```
PC_jr <= reg_read_val_1; -- PC_jr
```

```
pc_next <= PC_jr when (JRControl='1') else PC_4beqj; -- PC_next
```

I'll skip  
this part

(read from MIPS  
Arch chapter of  
Harris Harris  
textbook)

im\_shift\_1 <= imm\_ext(14 downto 0) & '0'; -- immediate shift 1

no\_sign\_ext <= (not im\_shift\_1) + x"0001";

PC\_beq <= (pc2 - no\_sign\_ext) when im\_shift\_1(15) = '1' else (pc2 + im\_shift\_1);

beq\_control <= branch and zero\_flag; -- beq control

PC\_4beq <= PC\_beq when beq\_control='1' else pc2; -- PC\_beq

jump\_shift\_1 <= instr(13 downto 0) & '0'; -- jump shift left 1

PC\_j <= pc2(15) & jump\_shift\_1; -- PC\_j

PC\_4beqj <= PC\_j when jump = '1' else PC\_4beq; -- PC\_4beqj

PC\_jr <= reg\_read\_data\_1; -- PC\_jr

pc\_next <= PC\_jr when (JRControl='1') else PC\_4beqj; -- PC\_next

SKIPPED!

ALU related ( left as exercise )

```
pc2 <= pc_current + x"0002";
```

```
Instruction_Memory: entity work.Instruction_Memory_VHDL
```

```
    port map      (      pc=>pc_current,      instruction => instr  );
```

```
control: entity work.control_unit_VHDL
```

```
    port map (reset=> reset,  opcode=> instr(15 downto 13),
```

```
    reg_dst=> reg_dst,  mem_to_reg => mem_to_reg,
```

```
    alu_op => alu_op,  jump => jump,  branch => branch,  mem_read => mem_read,
```

```
    mem_write => mem_write,  alu_src => alu_src,
```

```
    reg_write => reg_write,  sign_or_zero => sign_or_zero );
```

```
reg_write_dest <= "111" when reg_dst="10" else
```

```
    instr(6 downto 4) when reg_dst="01" else      instr(9 downto 7);
```

```
reg_read_addr_1 <= instr(12 downto 10); reg_read_addr_2 <= instr(9 downto 7);
```

```
register_file: entity work.register_file_VHDL port map
```

```
    ( clk => clk, rst => reset, reg_write_en => reg_write,
```

```
    reg_write_dest => reg_write_dest, reg_write_data => reg_write_data,
```

```
    reg_read_addr_1 => reg_read_addr_1, reg_read_data_1 => reg_read_data_1,
```

```
    reg_read_addr_2 => reg_read_addr_2, reg_read_data_2 => reg_read_data_2 );
```

```
read_data2 <= imm_ext when alu_src='1' else reg_read_data_2;
```

```
alu: entity work.ALU_VHDL port map (
```

```
    a => reg_read_data_1,  b => read_data2,
```

```
    alu_control => ALU_Control,  alu_result => ALU_out, zero => zero_flag );
```

ALU Control				
ALU op	Function	ALUcnt	ALU Operation	Instruction
11	XXXX	000	ADD	Addi,lw,sw
01	XXXX	001	SUB	BEQ
00	00	000	ADD	R-type: ADD
00	01	001	SUB	R-type: sub
00	02	010	AND	R-type: AND
00	03	011	OR	R-type: OR
00	04	100	slt	R-type: slt
10	XXXXXX	100	slt	i-type: slti




Already Discussed  
in Previous LectureLabMeet-1 1

1. Add :  $R[rd] = R[rs] + R[rt]$
2. Subtract :  $R[rd] = R[rs] - R[rt]$
3. And:  $R[rd] = R[rs] \& R[rt]$
4. Or :  $R[rd] = R[rs] | R[rt]$
5. SLT:  $R[rd] = 1$  if  $R[rs] < R[rt]$  else 0
6. Jr:  $PC = R[rs]$

RTH


register transfer  
notation

 


R-format

07 Code rs rt rd rd=1 Examples rs=2 rt=3

Name	Format	Example					Comments
		3 bits	3 bits	3 bits	3 bits	4 bits	
add	R	000	2010	011	001	0	add \$1,\$2,\$3
sub	R	000	2010	001	001	1	sub \$1,\$2,\$3
and	R	0	2	3	1	2	and \$1,\$2,\$3
or	R	0	2	3	1	3	or \$1,\$2,\$3
slt	R	0	2	3	1	4	slt \$1,\$2,\$3
jr	R	0	7	0	0	8	jr \$7
lw	I	4	2	1	7		lw \$1, 7 (\$2)
sw	I	5	2	1	7		sw \$1, 7 (\$2)
beq	I	6	1	2	7		beq \$1,\$2, 7
addi	I	7	2	1	7		addi \$1,\$2, 7
j	J	2	500				j 1000
jal	J	3	500				jal 1000
slti	I	1	2	1	7		slti \$1,\$2, 7

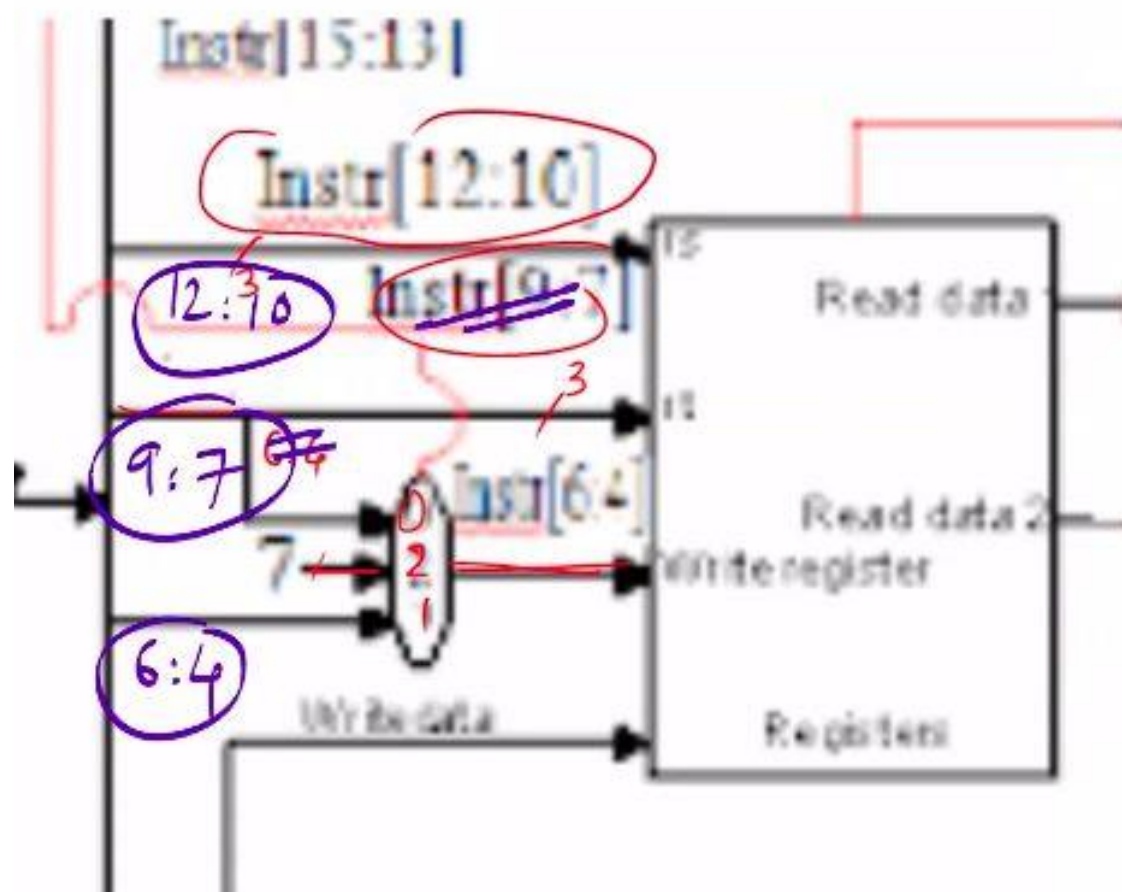
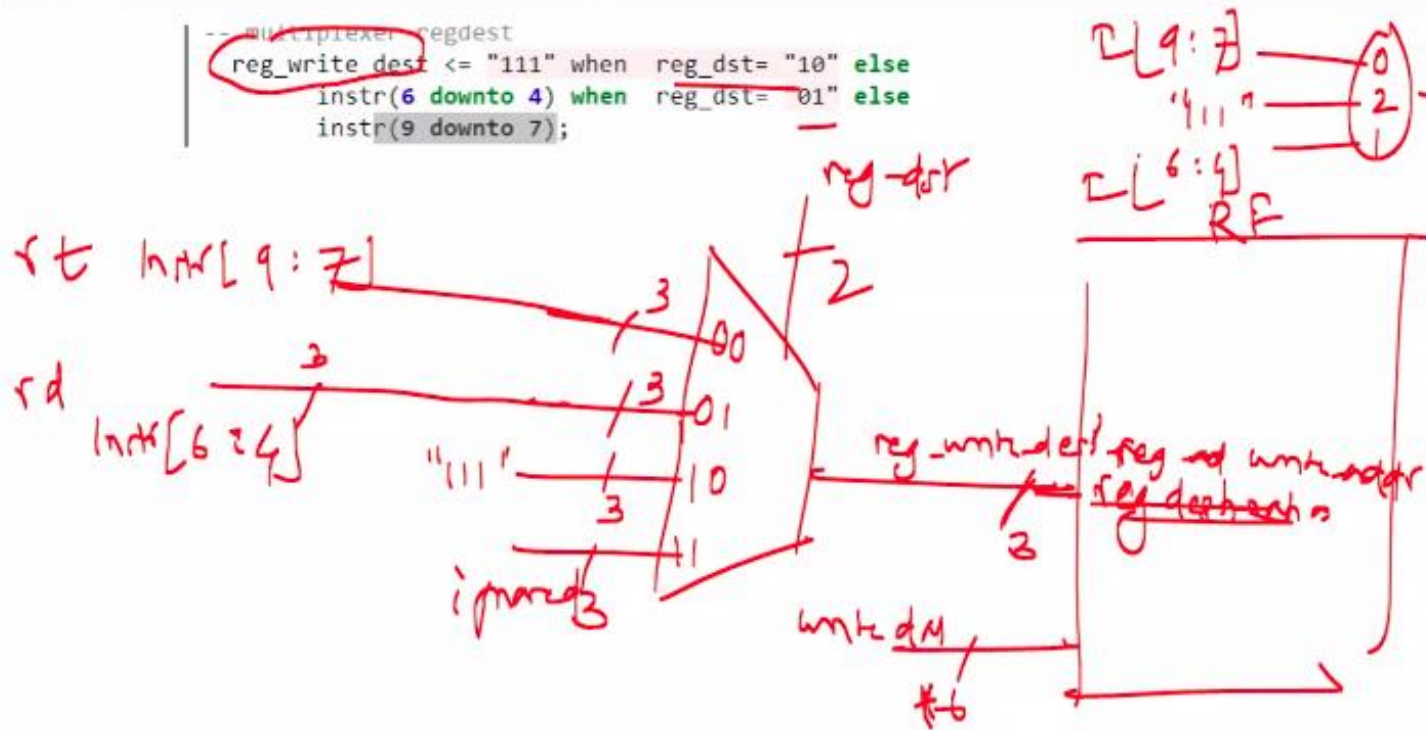
```
-- multiplexer regdest
reg_write_dest <= "111" when reg_dst = "10" else
  instr(6 downto 4) when reg_dst = "01" else
  instr(9 downto 7);
```



5. SLT:  $R[rd] = 1$  if  $R[rs] < R[rt]$  else 0

6. Jr:  $PC = R[rs]$

7. Lw:  $R[rt] = M[R[rs] + \text{SignExtImm}]$

8. Sw :  $M[R[rs] + \text{SignExtImm}] = R[rt]$

9. Beq : if( $R[rs] == R[rt]$ )  $PC = PC + 1 + \text{BranchAddr}$

10. Addi:  $R[rt] = R[rs] + \text{SignExtImm}$

11. J :  $PC = \text{JumpAddr}$

12. Jal :  $R[7] = PC + 2; PC = \text{JumpAddr}$

13. SLTI:  $R[rt] = 1$  if  $R[rs] < \text{imm}$  else 0

$\text{SignExtImm} = \{ 9\{\text{immediate}[6]\}, \text{imm} \}$

$\text{JumpAddr} = \{ (PC+1)[15:13], \text{address} \}$


$\text{BranchAddr} = \{ 7\{\text{immediate}[6]\}, \text{immediate}, 1'b0 \}$

notation

SLT:

set less than

 Reg # 7  $R[7]$  is used  
for holding return address







```

entity register_file_VHDL is port ( clk,rst: in std_logic; reg_write_en: in std_logic;
reg_write_dest: in std_logic_vector(2 downto 0);
reg_write_data: in std_logic_vector(15 downto 0); reg_read_addr_1: in std_logic_vector(2 downto 0);
reg_read_data_1: out std_logic_vector(15 downto 0); reg_read_addr_2: in std_logic_vector(2 downto 0);
reg_read_data_2: out std_logic_vector(15 downto 0)
);
end register_file_VHDL;
architecture Behavioral of register_file_VHDL is
    type reg_type is array (0 to 7) of std_logic_vector (15 downto 0);
    signal reg_array: reg_type;
begin
    process(clk,rst) begin
        if(rst='1') then .....
        elsif(rising_edge(clk)) then
            if(reg_write_en='1') then
                reg_array(to_integer(unsigned(reg_write_dest))) <= reg_write_data;
            end if;
        end if;
    end process;
    reg_read_data_1 <= x"0000" when reg_read_addr_1 = "000" else
                                                                    reg_array(to_integer(unsigned(reg_read_addr_1)));
    reg_read_data_2 <= x"0000" when reg_read_addr_2 = "000" else
                                                                    reg_array(to_integer(unsigned(reg_read_addr_2)));
end Behavioral;

```

 



 

6. Jr:  $PC = R[rs]$

7. Lw:  $R[rt] = M[R[rs] + \text{SignExtImm}]$

8. Sw :  $M[R[rs] + \text{SignExtImm}] = R[rt]$

9. Beq : if( $R[rs] == R[rt]$ )  $PC = PC + 1 + \text{BranchAddr}$

10. Addi:  $R[rt] = R[rs] + \text{SignExtImm}$


11. J :  $PC = \text{JumpAddr}$

12. Jal :  $R[7] = PC + 2; PC = \text{JumpAddr}$

 
13. SLTI:  $R[rt] = 1$  if  $R[rs] < \text{imm}$  else 0

$\text{SignExtImm} = \{ 9\{\text{immediate}[6]\}, \text{imm} \}$

$\text{JumpAddr} = \{ (PC+1)[15:13], \text{address} \}$




Sign Extended version of  
imm field

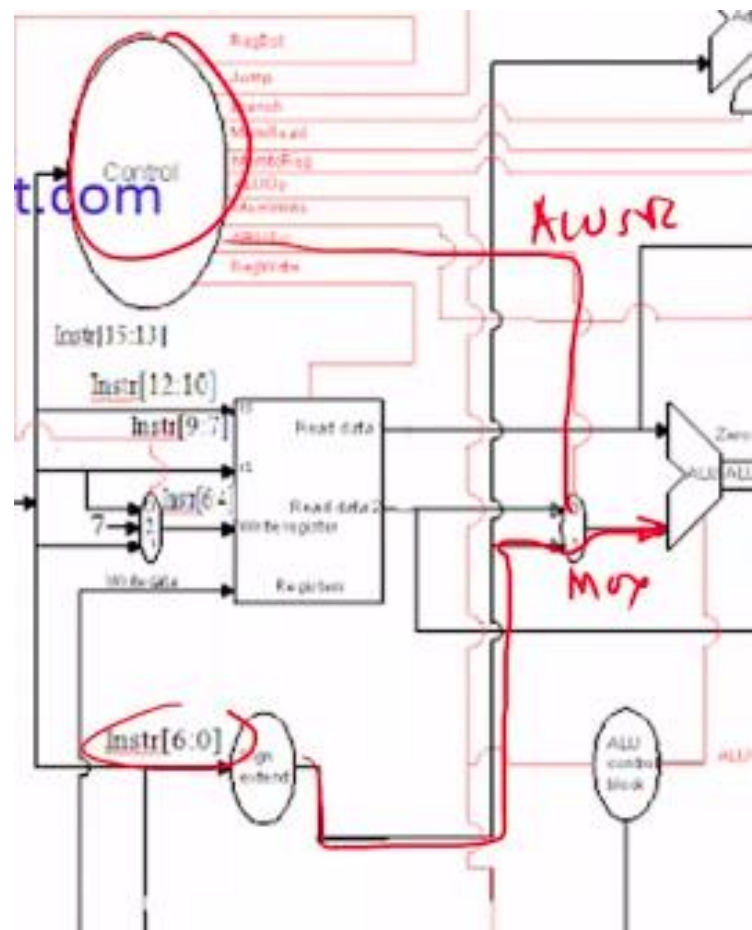

$\left[ \overleftrightarrow{\text{imm}} \right]_{6:0}$
 
```
-- sign extend
tmp1 <= (others => instr(6));
sign_ext_im <= tmp1 & instr(6 downto 0);
zero_ext_im <= "000000000" & instr(6 downto 0);
imm_ext <= sign_ext_im when sign_or_zero='1' else zero_ext_im;
```




```
Transcript
# 18-02-2021 13:29 <DIR> work
# 3 File(s) 26,372 bytes
# 3 Dir(s) 140,959,760,384 bytes free
VSIOM 16> vcom cpu_f4s.vhdl
# Model Technology ModelSim - Intel FPGA Edition vcom 10.5b Compiler 2016.10 Oct 5 2016
# Start time: 14:55:17 on Feb 18,2021
# vcom -reportprogress 300 cpu_f4s.vhdl
# -- Loading package STANDARD
# -- Loading package TEXTIO
# -- Loading package std_logic_1164
# -- Loading package NUMERIC_STD
# -- Compiling entity Data_Memory_VHDL
# -- Compiling architecture Behavioral of Data_Memory_VHDL
# -- Loading package std_logic_arith
# -- Loading package STD_LOGIC_SIGNED
# -- Compiling entity ALU_VHDL
# -- Compiling architecture Behavioral of ALU_VHDL
# -- Compiling entity ALU_Control_VHDL
# -- Compiling architecture Behavioral of ALU_Control_VHDL
# -- Compiling entity register_file_VHDL
# -- Compiling architecture Behavioral of register_file_VHDL
# -- Compiling entity control_unit_VHDL
# -- Compiling architecture Behavioral of control_unit_VHDL
# -- Compiling entity Instruction_Memory_VHDL
# -- Compiling architecture Behavioral of Instruction_Memory_VHDL
# -- Compiling entity MIPS_VHDL
# -- Compiling architecture Behavioral of MIPS_VHDL
# -- Loading entity Instruction_Memory_VHDL
# -- Loading entity control_unit_VHDL
# -- Loading entity register_file_VHDL
# -- Loading entity ALU_Control_VHDL
# -- Loading entity ALU_VHDL
# -- Loading entity Data_Memory_VHDL
# -- Compiling entity tb_MIPS_VHDL
# -- Compiling architecture behavior of tb_MIPS_VHDL
# End time: 14:55:17 on Feb 18,2021, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
VSIOM 17> |
```



```
# -- Compiling entity register_file_VHDL
# -- Compiling architecture Behavioral of register_file_VHDL
# -- Compiling entity control_unit_VHDL
# -- Compiling architecture Behavioral of control_unit_VHDL
# -- Compiling entity Instruction_Memory_VHDL
# -- Compiling architecture Behavioral of Instruction_Memory_VHDL
# -- Compiling entity MIPS_VHDL
# -- Compiling architecture Behavioral of MIPS_VHDL
# -- Loading entity Instruction_Memory_VHDL
# -- Loading entity control_unit_VHDL
# -- Loading entity register_file_VHDL
# -- Loading entity ALU_Control_VHDL
# -- Loading entity ALU_VHDL
# -- Loading entity Data_Memory_VHDL
# -- Compiling entity tb_MIPS_VHDL
# -- Compiling architecture behavior of tb_MIPS_VHDL
# End time: 14:55:17 on Feb 18, 2021, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
VSI17> vsim tb_MIPS_VHDL
# End time: 14:56:15 on Feb 18, 2021, Elapsed time: 1:25:27
# Errors: 0, Warnings: 26
# vsim tb_MIPS_VHDL
# Start time: 14:56:15 on Feb 18, 2021
# Loading std.standard
# Loading std.textio(body)
# Loading ieee.std_logic_1164(body)
# Loading work.tb_mips_vhdl(body)
# Loading ieee.std_logic_arith(body)
# Loading ieee.std_logic_signed(body)
# Loading ieee.numeric_std(body)
# Loading work.mips_vhdl(body)
# Loading work.instruction_memory_vhdl(body)
# Loading work.control_unit_vhdl(body)
# Loading work.register_file_vhdl(body)
# Loading work.alu_control_vhdl(body)
# Loading work.alu_vhdl(body)
# Loading work.data_memory_vhdl(body)

VSI18>
```



 

Name	Value
pc_current[15:0]	000e
reg_array[0:7]	[0001, 0000, 0003,
[0]	0001
[1]	0000
[2]	0003
[3]	000b
[4]	003e
[5]	0006
[6]	0007
[7]	0008
clk	1
mem_access_addr[15:0]	0000
mem_write_data[15:0]	0000
mem_write_en	0
mem_read	0
mem_read_data[15:0]	0000
i	80000000

